

## AD7224 Provides Programmable Voltages Over Varying Ranges

by Mike Byrne

This application note discusses some uses of the AD7224 in providing programmable output voltages over varying ranges. The AD7224 is a monolithic, voltage-mode CMOS DAC with output buffer amplifier housed in a 0.3 inch wide, 18-pin DIP.

The circuit of Figure 1a shows a common configuration for a potentiometer with the output voltage,  $V_{OUT}$ , varying from  $V_A$  to  $V_B$ . This output voltage is varied using the variable resistor VR1. The function performed by this circuit can be implemented using the circuit of Figure 1b. This circuit uses the AD7224 and just three external components to give a programmable output voltage varying from  $V_X$  to  $V_Y$ .

 


Figure 1a.

 


Figure 1b.

The operation of the circuit depends upon the principle that all the current which flows into the  $V_{REF}$  input of the AD7224 will flow out of AGND. Therefore, although the current flowing into the  $V_{REF}$  input will vary (because of varying input impedance with code) the current flowing through R2 will always remain constant. In practice some current flowing into the  $V_{REF}$  input will "leak" away from AGND. This leakage current varies with digital code. This variation is typically of the order of  $3\mu\text{A}$  which represents an error of only 0.05% since the typical current which flows through the zener is  $6\text{mA}$ . For example, if  $V_X$  is biased at  $2\text{V}$ , with  $R2 = 330\Omega$  the variation of  $V_X$  with digital code is typically less than  $1\text{mV}$ .

An additional separate current, which does not flow into the  $V_{REF}$  input, flows from  $V_{DD}$  through internal circuitry and out of AGND. This current is independent of code and therefore does not cause variations in  $V_X$  over the input code range. It is in the range  $50\mu\text{A}$  to  $150\mu\text{A}$  and is dependent upon the  $(V_Y - V_X)$  voltage; the lower the  $(V_Y - V_X)$  voltage the smaller the current. It does mean that  $V_X$ , and hence  $V_Y$ , will be slightly larger than one would expect based on the current flowing through R1. For example, with  $R2 = 330\Omega$ ,  $V_{DD} = +12\text{V}$  and  $(V_Y - V_X) = +6.1\text{V}$  it was found that  $V_X$  was  $43\text{mV}$  larger than expected. Under the same conditions except  $(V_Y - V_X) = 3.3\text{V}$ ,  $V_X$  was  $22\text{mV}$  larger than expected. In either case the increased  $V_X$  can easily be adjusted for by reducing R2.

The zener diode, D1, must be biased so that the current variation through it will not significantly affect its zener voltage. The worst case variation for the circuit of Figure 1b is  $1\text{mA}$  over the input code range but typically this is less than  $500\mu\text{A}$ . The total variation on  $V_Y$ , including the effect of the variation on  $V_X$ , was found to be less than  $2\text{mV}$ . This was for various values of D1 with  $V_X = 2\text{V}$  and  $R2 = 330\Omega$ .

The circuit of Figure 1b is not as flexible as that of 1a and a number of limitations exist.  $V_Y$  must be at least  $4\text{V}$  below the  $V_{DD}$  supply voltage to ensure correct operation of the AD7224. Additionally,  $V_Y$  must always be positive with respect to  $V_X$  and in turn,  $V_X$  must always be positive with



 


Figure 3.  $V_O$  Versus Digital Code

Another configuration, using the AD7224 with the LM10 and giving a similar output voltage range, is outlined in Figure 4. In this case A1 is used to drive the  $V_{REF}$  of the AD7224 directly. A2 is then used in conjunction with a series pass transistor, T1, to provide current boosting with up to 100mA being provided across  $R_L$ . The output voltage range with the component values given in Figure 4, is, once again, 1V to 10V. The positive supply and return

paths for the transistor and load have to be kept separate from the supply paths for the rest of the circuit to avoid errors caused by resistive drops with large currents flowing. Varying the ratios of R6 to R5 and R8 to R7 changes the output voltage range with the expression for the output voltage,  $V_O$ , being

$$V_O = V_R \cdot \frac{(1 + G1) \cdot (1 + G2)}{(1 + G1 \cdot D)}$$

$$\text{where } G1 = R6/R5$$

$$G2 = R8/R7$$

and D is a fractional representation of the digital word in the DAC register.

In both the circuit of Figure 2 and Figure 4 the AD7224 is shown operating from dual supplies (i.e.,  $V_{SS} = -5V$ ). The reason for this is that the AD7224 loses its output sink capability with output voltages near AGND when operated in single supply. In dual supply operation it maintains a 400 $\mu$ A output sink capability over the entire output voltage range. Resistor values for R3 in Figure 2 and R5 in Figure 4 should be chosen so that this 400 $\mu$ A output sink current is not exceeded. If single supply operation is required, the  $V_{SS}$  of the AD7224 can be tied to DGND with the AGND of the AD7224 (and all other AGND points in the circuit) biased to 2V. In this case the output will again have its full sink capability over the output range.

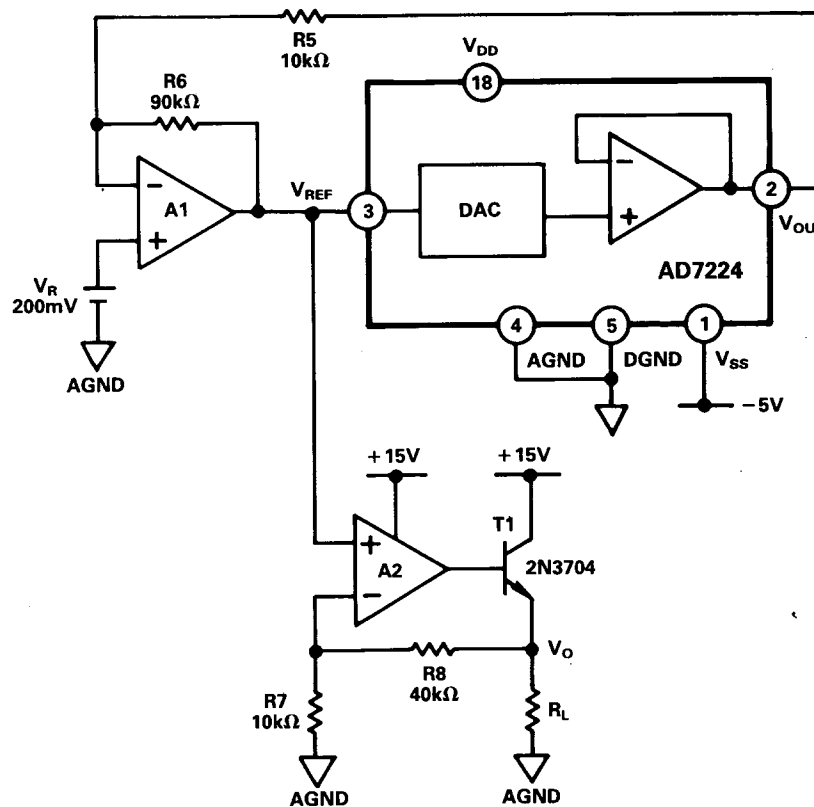


Figure 4. Current-Boost Configuration